

Parametric Analysis

LTspice DC sweep of the lower divider resistor.

What this demonstrates

R2 is defined as the swept parameter. The `.step param Rvar 500 5k 500`` command varies it from 500 Ω to 5 k Ω , and the plotted V(out) response increases accordingly.

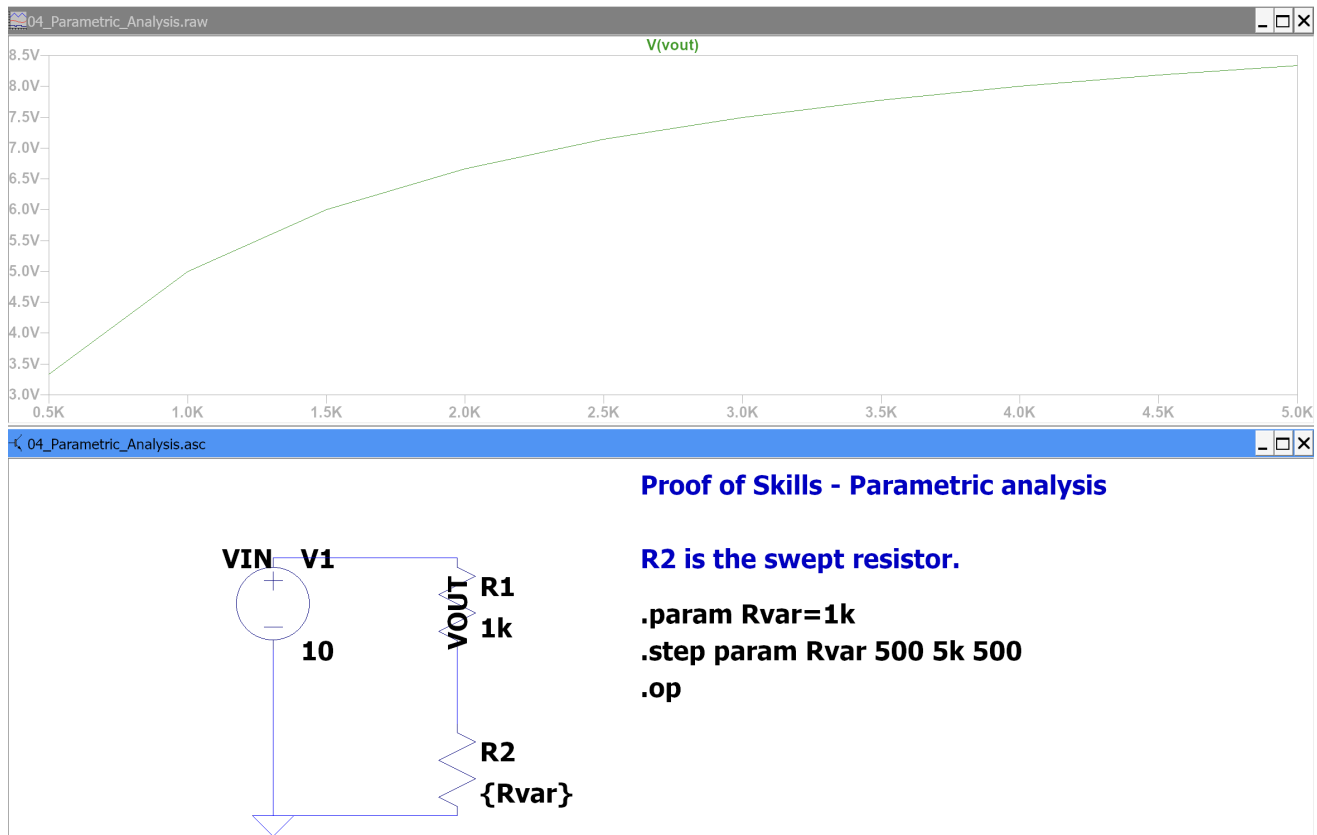


Figure 1. Parametric schematic, stepping command, and V(out) response.