

RC Low-Pass AC Analysis

LTspice frequency-response analysis of an RC low-pass circuit.

What this demonstrates

The capture includes the `.ac dec 100 10 100k` sweep, magnitude and phase Bode curves, and a cursor at 1 kHz showing approximately -3.006 dB and -44.97° .

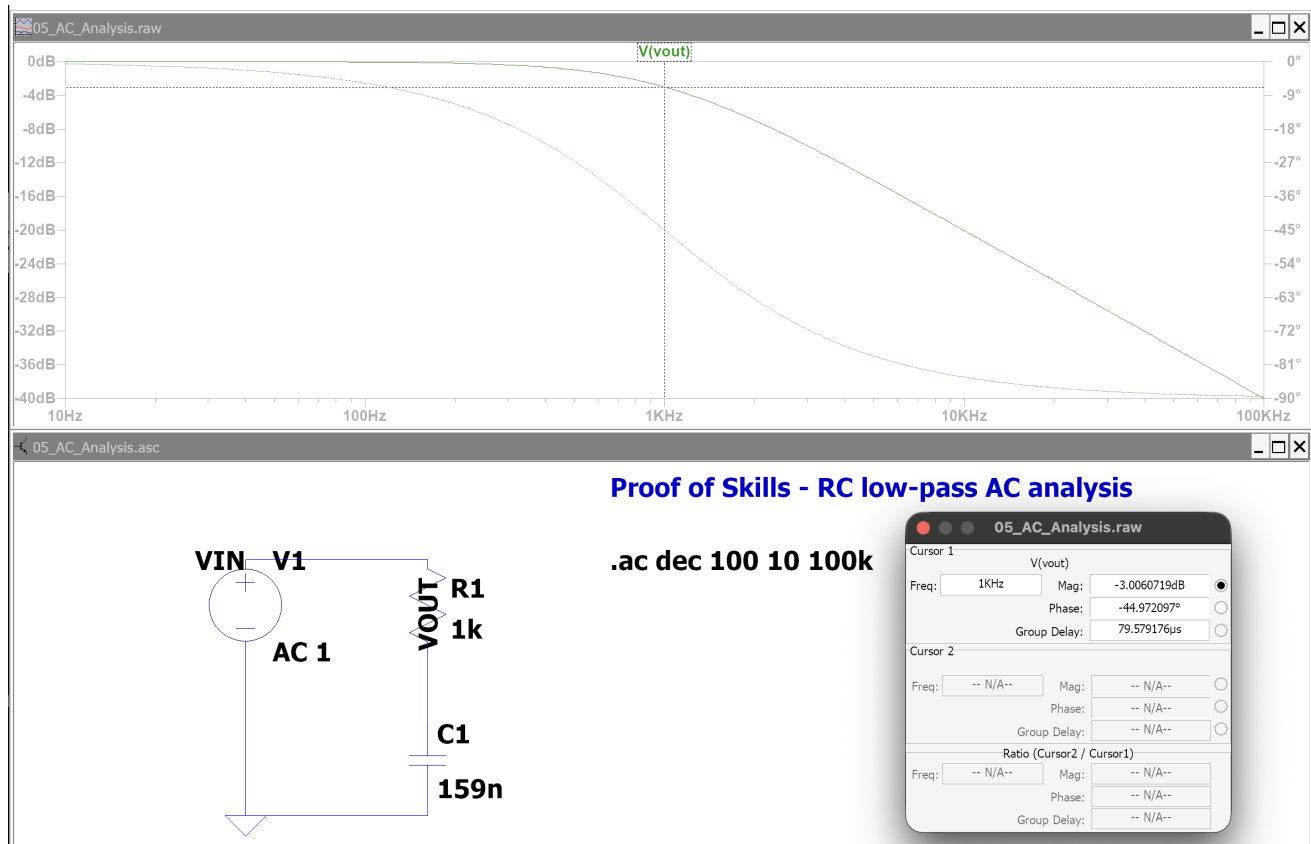


Figure 1. RC low-pass schematic and AC magnitude/phase response.