

Transient Analysis

LTspice time-domain analysis of a sinusoidal voltage-divider output.

What this demonstrates

The capture includes the `.tran 0 5m`` directive, the 1 kHz sinusoidal source, the divider schematic, and the resulting $V(out)$ waveform over 0–5 ms.

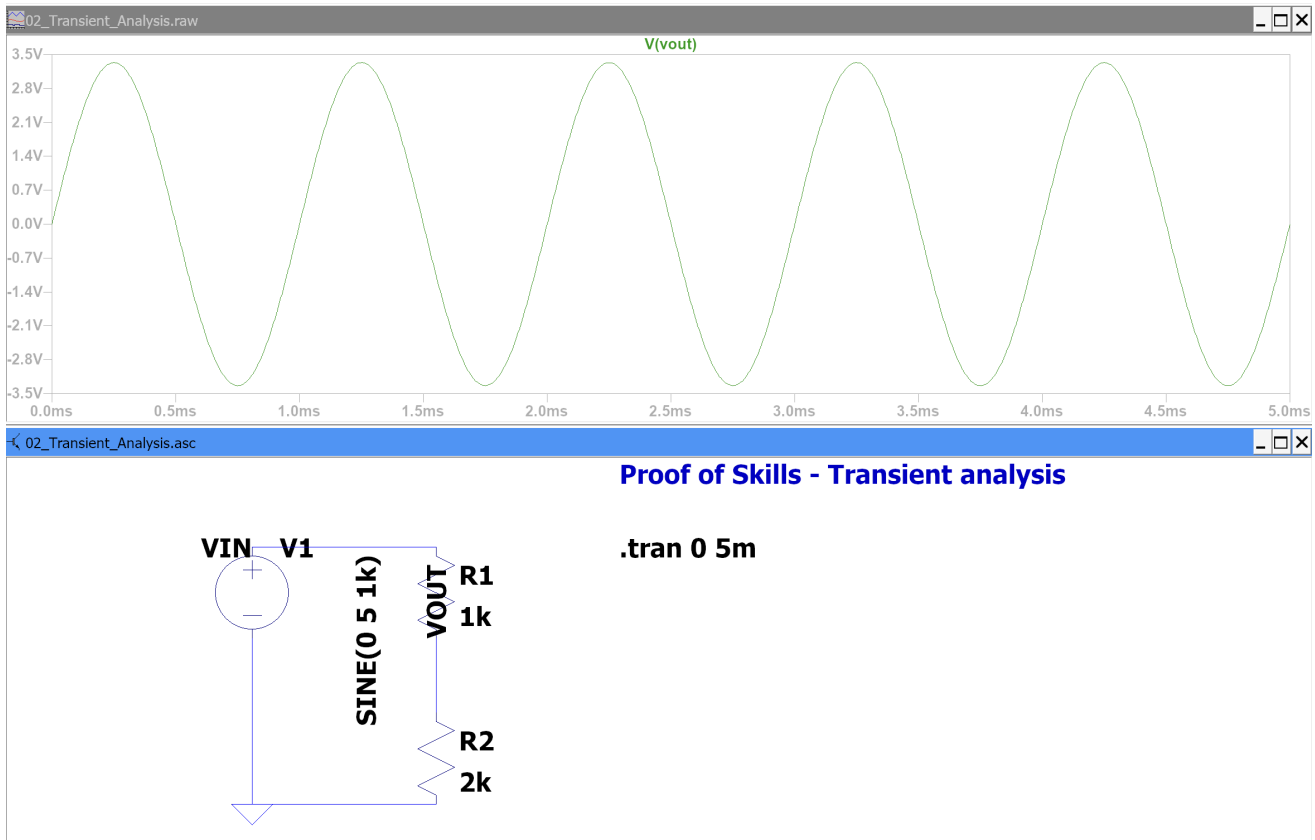


Figure 1. LTspice transient setup and $V(out)$ waveform.